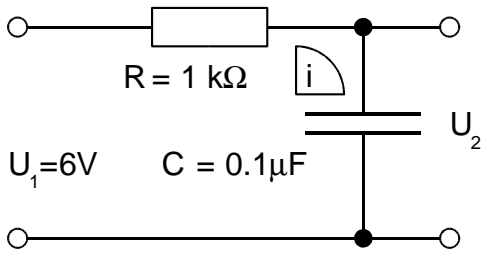


1.



U

- a: $f_A = 2000 \text{ Hz}$
 $X_A = \dots \Omega$
 $Z_A = \dots \Omega$
 $U_{2A} = \dots \text{ V}$
- b: $I = \dots \text{ A}$
- c: $U_2 \Rightarrow f$ diagram

$$C = 0.1 \mu\text{F} = 0.1 \cdot 10^{-6} \text{ F} = 10^{-7} \text{ F}$$

$$R = 1 \text{ k}\Omega = 1 \cdot 10^3 \Omega = 10^3 \Omega$$

a:

$$X_A = \frac{1}{2\pi \cdot f_A \cdot C} = \frac{1}{2\pi \cdot 2000 \cdot 10^{-7}} = 795.77 \Omega$$


$$Z_A = \sqrt{R^2 + X_A^2} = \sqrt{(10^3)^2 + (795.77)^2} = 1278 \Omega$$

$$U_{2A} = i \cdot X_A$$


b: $i = \frac{U}{Z_A} = \frac{6}{1278} = 4.695 \cdot 10^{-3} \text{ A} = 4.695 \text{ mA}$

a: $U_{2A} = i \cdot X_A = 4.695 \cdot 10^{-3} \cdot 795.77 = 3.736 \text{ V}$

c:

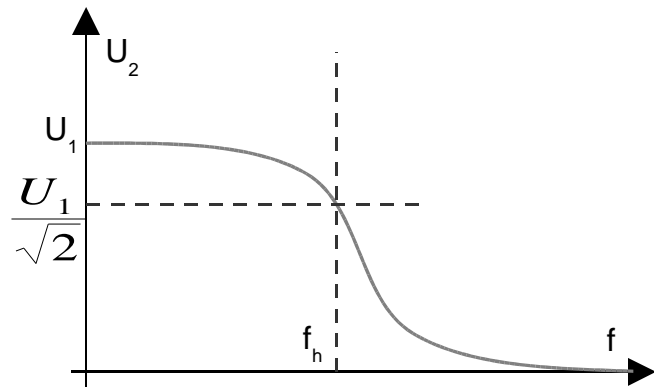

2

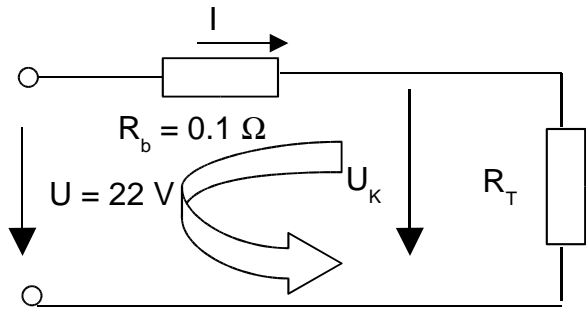


- a: $I_1 = 20\text{A}$
 $R_{T1} = \dots \dots \dots \Omega$
 $U_{K1} = \dots \dots \dots \Omega$
- b: $I_2 = 10\text{A}$
 $R_{T2} = \dots \dots \dots \Omega$
 $U_{K2} = \dots \dots \dots \Omega$
- c: $I_Z = \dots \dots \dots \Omega$
- d: $U_k \Rightarrow I$, képlet

a: $I_1 = \frac{U}{R_b + R_{T1}} \Rightarrow R_b + R_{T1} = \frac{U}{I_1} \Rightarrow R_{T1} = \frac{U}{I_1} - R_b = \frac{22}{20} - 0.1 = 1\Omega$
 $U_{K1} = I_{T1} \cdot R_{T1} = 20 \cdot 1 = 20V$


b: $I_2 = \frac{U}{R_b + R_{T2}} \Rightarrow R_b + R_{T2} = \frac{U}{I_2} \Rightarrow R_{T2} = \frac{U}{I_2} - R_b = \frac{22}{10} - 0.1 = 2.1\Omega$
 $U_{K2} = I_{T2} \cdot R_{T2} = 10 \cdot 2.1 = 21V$

c: zárlat van akkor, ha $R_T = R_{TZ} = 0$ $I_Z = \frac{U}{R_b + R_{TZ}} = \frac{U}{R_b + 0} = \frac{U}{R_b} = \frac{22}{0.1} = 220A$

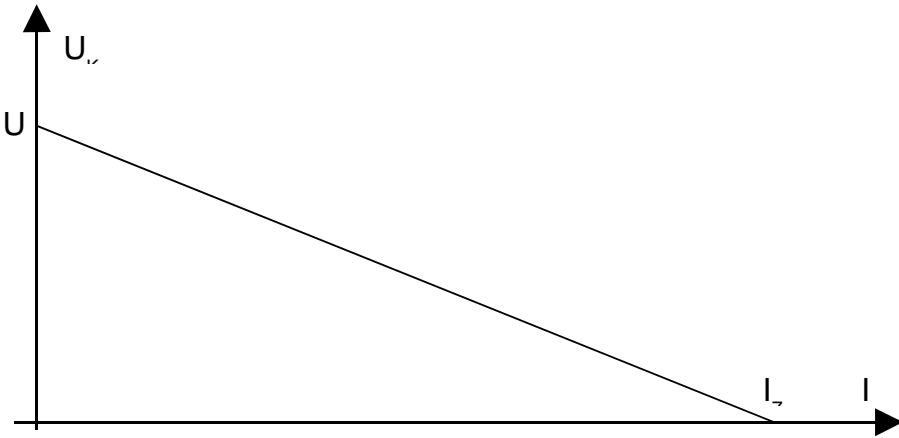d: A Kirchoff huroktörvényből (lásd nyílirány): $U - U_k - I \cdot R_b = 0 \Rightarrow U_k = U - I \cdot R_b$



3

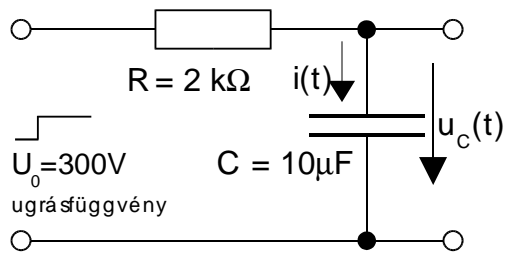

- a: az időállandó $\tau = \dots \dots \dots s$
- b: időfüggvény $u_C(t) = \dots \dots \dots$
- c: ábrázolás: $i(t)$
- d: $t_1 = 10ms$
 $u_{C1} = \dots \dots \dots V$
 $i_1 = \dots \dots \dots A$

$R = 2k\Omega = 2 \cdot 10^3 \Omega = 2000\Omega$
 $C = 10\mu F = 10 \cdot 10^{-6} F = 10^{-5} F$


a: $\tau = R \cdot C = 2000 \cdot 10^{-5} = 2 \cdot 10^{-2} s = 0.02s$

b: ha $t < 0$, akkor $u_C = 0$.

Ha $0 \leq t$, akkor $u_C(t) = U_0 - i(t) \cdot R$ (lásd Kirchoff huroktörvény 2. feladat)

$$i(t) = \frac{U_0}{R} \cdot e^{-\frac{t}{\tau}} \Rightarrow u_C(t) = U_0 - \frac{U_0}{R} \cdot e^{-\frac{t}{\tau}} \cdot R = U_0 - U_0 \cdot e^{-\frac{t}{\tau}} = U_0 \cdot \left(1 - e^{-\frac{t}{\tau}}\right)$$

c:

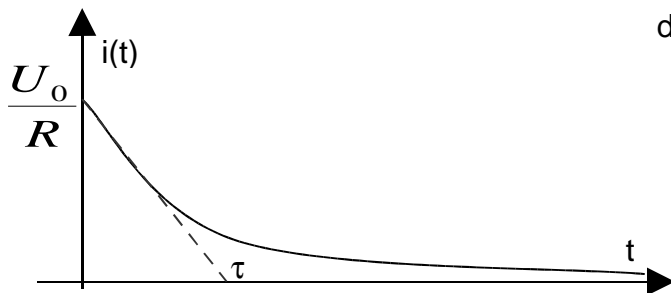

d: $t_1 = 10ms = 10 \cdot 10^{-3} s = 10^{-2} s$

$$u_{C1} = U_0 \cdot \left(1 - e^{-\frac{t_1}{\tau}}\right) = 300 \cdot \left(1 - e^{-\frac{10^{-2}}{2 \cdot 10^{-2}}}\right) = 300 \cdot \left(1 - e^{-\frac{1}{2}}\right) = 300 \cdot \left(1 - \frac{1}{\sqrt{e}}\right) \approx 118V$$

$$i_1 = \frac{U_0}{R} \cdot e^{-\frac{t_1}{\tau}} = \frac{300}{2000} \cdot e^{-\frac{10^{-2}}{2 \cdot 10^{-2}}} = \frac{3}{20} \cdot \frac{1}{\sqrt{e}} \approx 0.09A$$