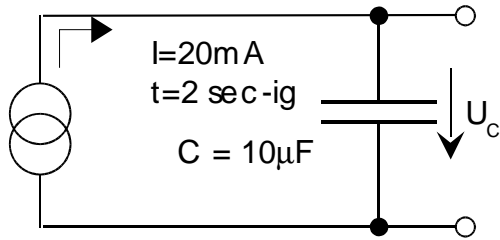


V

1.



$Q = \dots\dots\dots As$
 $W_C = \dots\dots\dots J$
 $U_C = \dots\dots\dots V$
 $U_C(t) = \dots\dots\dots, \text{ábrázolás}$

$I = 20mA = 20 \cdot 10^{-3} A = 2 \cdot 10^{-2} A = 0.02$


$C = 10\mu F = 10 \cdot 10^{-6} F = 10^{-5} F$


$Q = I \cdot t = 0.02 \cdot 2 = 0.04 As$

$U_C = \frac{Q}{C} = \frac{0.04}{10^{-5}} = 4000V$

$W_C = \frac{1}{2} Q \cdot U = \frac{1}{2} \frac{Q^2}{C} = \frac{1}{2} \frac{0.04^2}{10^{-5}} = 80J$

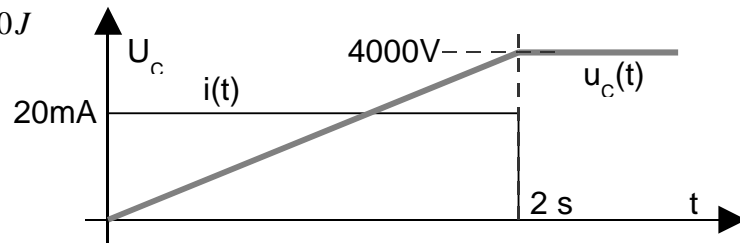$U_C(t) = \frac{Q}{C} = \frac{I \cdot t}{C} = \frac{I}{C} t \Rightarrow$



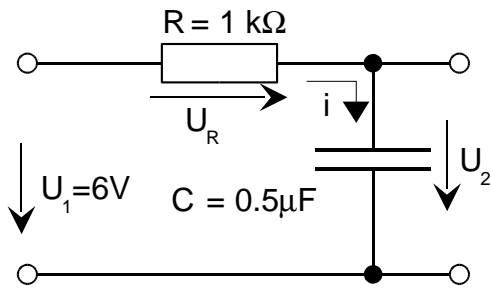

2.
 $f_h = \dots \text{Hz}$
 $f = 1.5 f_h$ esetén
 $U_2 = \dots \text{V}$
 $\varphi_{12} = \dots U_1$ és U_2 között
 $I = \dots \text{A}$
 vektorabra

$R = 1 \text{k}\Omega = 10^3 \Omega$

$C = 0.5 \mu\text{F} = 0.5 \cdot 10^{-6} \text{F} = 5 \cdot 10^{-7} \text{F}$

$f_h = \frac{1}{2\pi \cdot RC} = \frac{1}{2\pi \cdot 10^3 \cdot 5 \cdot 10^{-7}} = 318.3 \text{Hz}$

$f = 1.5 \cdot f_h = 477.46 \text{Hz}$

$X_C = \frac{1}{2\pi \cdot f \cdot C} = \frac{1}{2\pi \cdot 477.46 \cdot 5 \cdot 10^{-7}} = 666.66 \Omega$


$Z = \sqrt{R^2 + X_C^2} = \sqrt{(10^3)^2 + 666.66^2} = 1202 \Omega$

$I = \frac{U}{Z} = \frac{6}{1202} = 0.00499 = 4.99 \cdot 10^{-3} \text{A} \approx 5 \text{mA}$


$U_2 = X_C \cdot I = 666.66 \cdot 4.99 \cdot 10^{-3} = 3.328 \text{V}$

$\text{tg}(\varphi_{12}) = \frac{U_R}{U_2}$

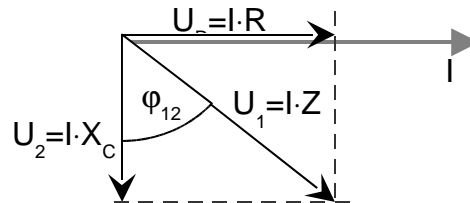$\varphi_{12} = \arctg\left(\frac{U_R}{U_2}\right) = \arctg\left(\frac{I \cdot R}{I \cdot X_C}\right) = \arctg\left(\frac{R}{X_C}\right) = \arctg\left(\frac{10^3}{666.66}\right) = 56.31^\circ$



3.

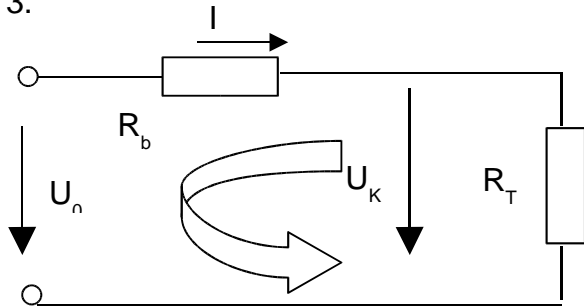

$I_1=4A \Rightarrow U_{K1}=12V$
 $U_{K2}=10V \Rightarrow I_2=14A$
 $U_0=.....V$
 $R_b=.....\Omega$
 $R_{T1}=.....\Omega$
 $I_z=.....A$
 Ábrázolandó U_K I függvényében + képlet

Kirchoff huroktörvény: $U_0 - I \cdot R_b - U_K = 0 \Rightarrow U_0 = I \cdot R_b + U_K$

$$\begin{aligned}
 I.: U_0 &= I_1 \cdot R_b + U_{K1} & \Rightarrow & \quad I.: U_0 = 4 \cdot R_b + 12 \\
 II.: U_0 &= I_2 \cdot R_b + U_{K2} & \Rightarrow & \quad II.: U_0 = 14 \cdot R_b + 10 \Rightarrow U_0 = 4 \cdot R_b + 12 = 14 \cdot R_b + 10 \Rightarrow \\
 & & \Rightarrow & \quad 2 = 10 \cdot R_b \Rightarrow R_b = 0.2\Omega
 \end{aligned}$$

$U_0 = 4 \cdot R_b + 12 = 4 \cdot 0.2 + 12 = 12.8V$ (ellenőrzés: $U_0 = 14 \cdot R_b + 10 = 12.8V$)

$$R_{T1} = \frac{U_{K1}}{I_1} = \frac{12}{4} = 3\Omega$$

I_z zárlati áram, amikor $R_T = 0$:

$$I_z = \frac{U_0}{R_b + R_T} = \frac{U_0}{R_b + 0} = \frac{U_0}{R_b} = \frac{12.8}{0.2} = 64A$$

$U_K(I)$: Kirchoff huroktörvény: $U_0 - I \cdot R_b - U_K = 0 \Rightarrow U_0 - I \cdot R_b = U_K$

